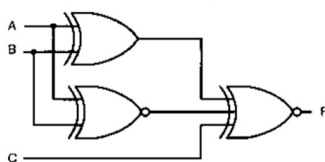


Q.12

Question: For the output **F** to be 1 in the logic circuit shown, the input combination should be:



Options:

- (A) $A = 1, B = 1, C = 0$ (C) $A = 0, B = 1, C = 0$
(B) $A = 1, B = 0, C = 0$ (D) $A = 0, B = 0, C = 1$

Detailed Solution

We analyze the circuit step by step:

$$X = A \oplus B \quad (\text{XOR gate output})$$

$$Y = (A \oplus B)' \quad (\text{XNOR gate output})$$

$$Z = X + Y \quad (\text{OR gate output})$$

$$F = Z \oplus C \quad (\text{Final XOR with input } C)$$

Option (A): $A = 1, B = 1, C = 0$

$$X = 1 \oplus 1 = 0$$

$$Y = (1 \oplus 1)' = 1$$

$$Z = 0 + 1 = 1$$

$$F = 1 \oplus 0 = 1 \quad \checkmark$$

Option (B): $A = 1, B = 0, C = 0$

$$X = 1 \oplus 0 = 1$$

$$Y = (1 \oplus 0)' = 0$$

$$Z = 1 + 0 = 1$$

$$F = 1 \oplus 0 = 1 \quad \checkmark$$

Option (C): $A = 0, B = 1, C = 0$

$$X = 0 \oplus 1 = 1$$

$$Y = (0 \oplus 1)' = 0$$

$$Z = 1 + 0 = 1$$

$$F = 1 \oplus 0 = 1 \quad \checkmark$$

Option (D): $A = 0, B = 0, C = 1$

$$X = 0 \oplus 0 = 0$$

$$Y = (0 \oplus 0)' = 1$$

$$Z = 0 + 1 = 1$$

$$F = 1 \oplus 1 = 0 \quad \times$$

Conclusion

Options (A), (B), and (C) all result in $F = 1$.

Correct Answers: (A), (B), and (C)